

BASICS OF ELECTRICITY

SEMINAR: Future challenges and trends in HCI - Physical Computing



MADHURIMA VARUGHESE

23-May-2014

AGENDA



Introduction

Basics of Electricity

Components of Electrical
Circuits

Conclusion



INTRODUCTION

Transduction

INTRODUCTION

✚ Transduction

➤ Conversion of one form of energy into another.




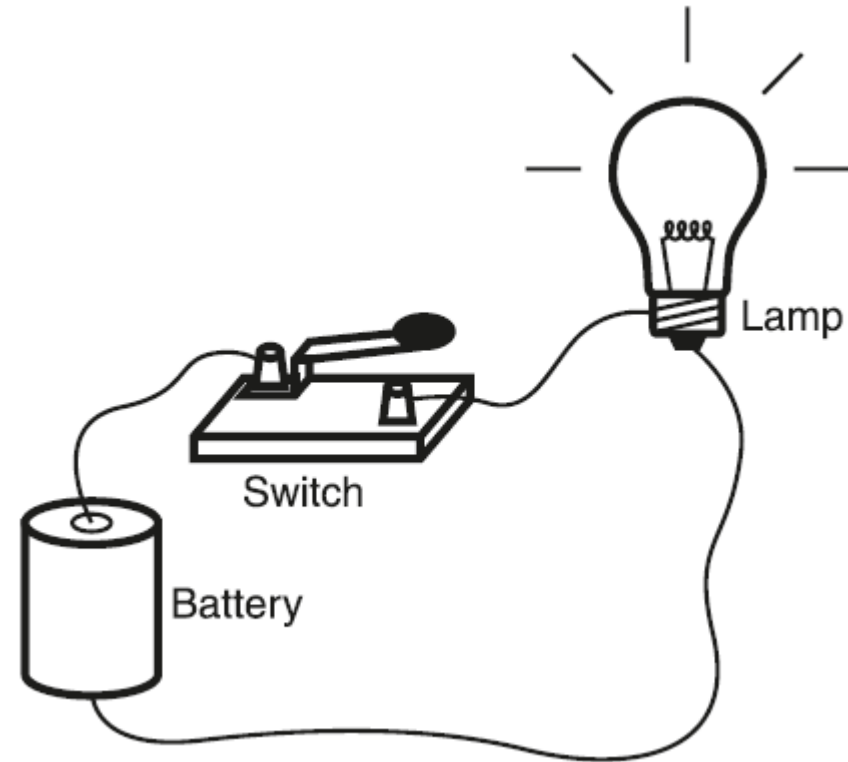


BASICS OF ELECTRICITY


Glossary of Terms, Ohm's law, Flow of Electricity

ELECTRICITY BASICS — GLOSSARY

- ✚ Power, Ground & Conductor
- ✚ Circuit
- ✚ Voltage, Current & Resistance
- ✚ DC & AC
- ✚ Short circuit 
- ✚ Electrical power/ Wattage



ELECTRICITY BASICS – VOLT, OHM, AMP

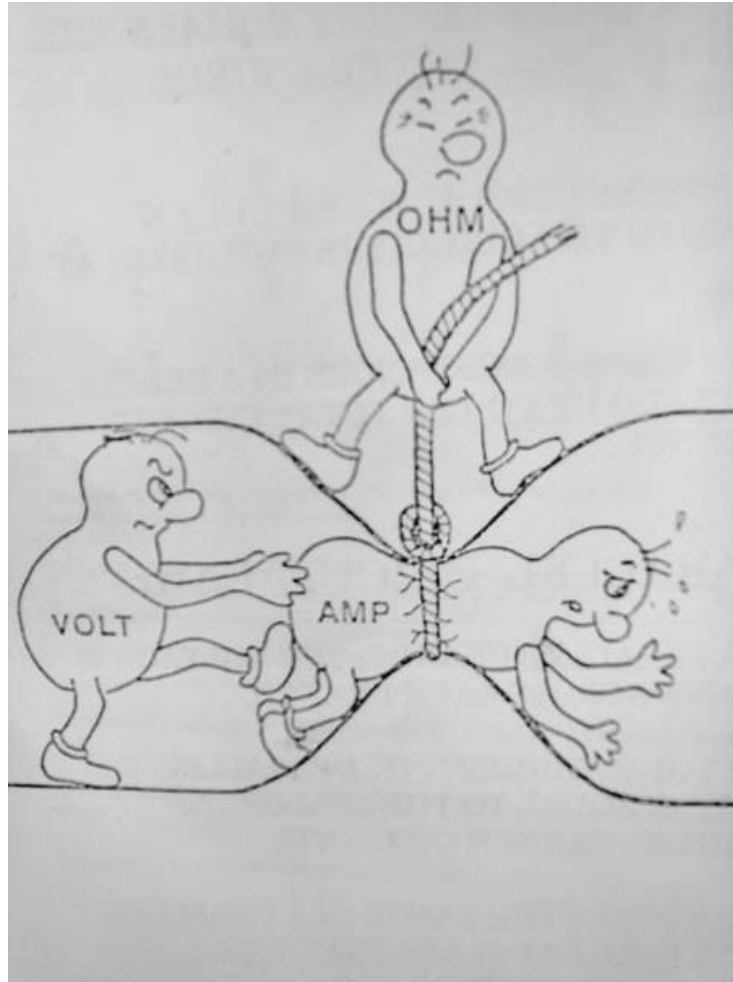

References:[4]

ELECTRICITY BASICS — OHM'S LAW




$$V = I * R,$$

where





V = Voltage expressed in volts,

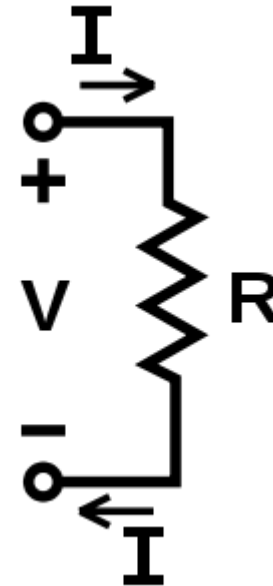I = Current expressed in amperes

R = Resistance expressed in Ohms



ELECTRICITY BASICS — FLOW OF ELECTRICITY

	High Current	Low Current
High Voltage	 <p>By Johnny Albert10 [Public domain], via Wikimedia Commons</p>	 <p>By Tomaszp [CC-BY-SA-3.0], via Wikimedia Commons</p>
Low Voltage	 <p>USGS image, via Wikimedia Commons</p>	 <p>By User:Ruhfisch [GFDL] via Wikimedia Commons</p>

References:[2]


ELECTRICITY BASICS — FLOW OF ELECTRICITY

Properties of Electrical Energy:

- ✚ Electricity always favour the path of least resistance to ground
- ✚ All the electrical energy in a circuit must be used.

Types of Connection:

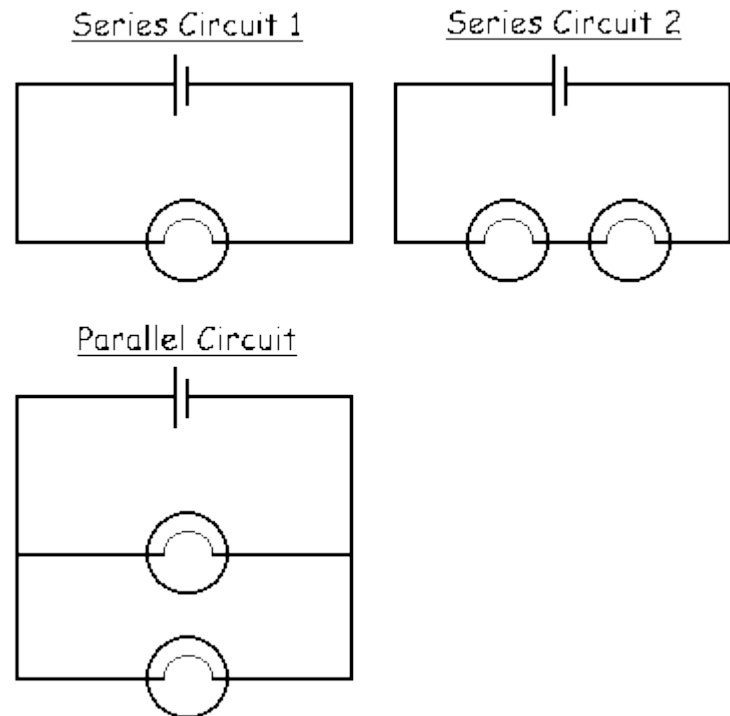
- ✚ Series connection
- ✚ Parallel connection



References:[3]

ELECTRICITY BASICS — FLOW OF ELECTRICITY

Short Circuit!!

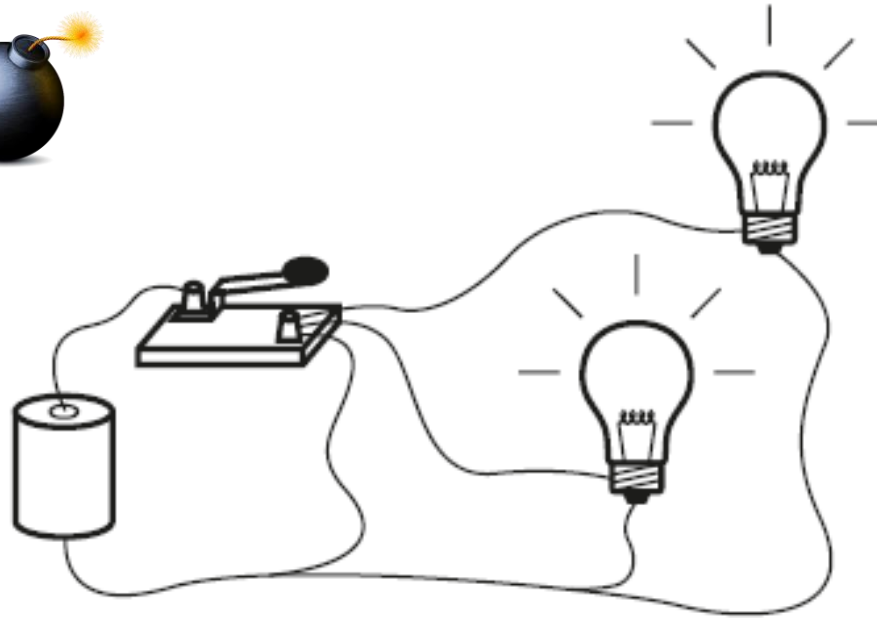

References:[3]



COMPONENTS OF ELECTRIC CIRCUITS

Switches, Resistors, Diodes and LEDs, Transistors and Relays, Multimeter

SWITCHES

- ✚ Pass or interrupt flow of electricity.

- ✚ Schematic Symbol:



- ✚ Rated by: Maximum voltage and current conducted

- ✚ Types:

- ✚ Normally Open(N.O) & Normally Closed(N.C)
- ✚ Momentary or Toggle



RESISTORS

- ✚ Reduce current flow within circuits.

- ✚ Convert electrical energy to heat.


- ✚ Schematic Symbol:



- ✚ Rated in: Ohms

✚ VARIABLE RESISTORS:

- ✚ Schematic Symbol:

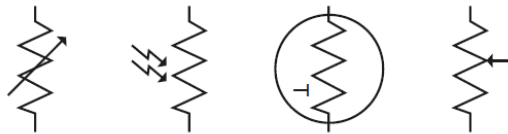

- ✚ E.g.: Thermistors, Photocells, Force-sensitive resistors, Potentiometer etc.



CAPACITORS

✚ When electricity flows into a capacitor, it stores up the charge. When the current is removed, the capacitor releases its charge until it's got no charge left.

✚ Schematic Symbol: 

✚ Rated by: Capacitance measured in Farads(F or mF or μF)



DIODES & LED'S


- ✚ Only allows electricity to flow in one direction and not the other.


- ✚ cathode (-), and the anode (+)

- ✚ Schematic Symbol: 

- ✚ Types: General-purpose, LED

- ✚ LED: Diode that also emits light in the process

- ✚ Schematic Symbol: 

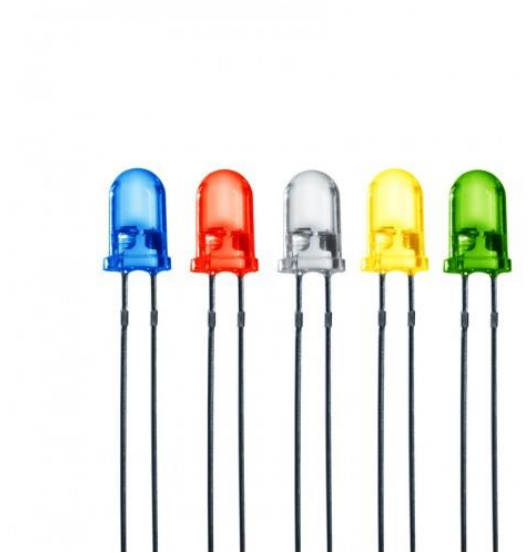

TRANSISTORS & RELAYS

✚ Switching devices (small switches that activate larger switches).



TRANSISTOR:

✚ Schematic Symbol:



RELAY

✚ Schematic Symbol:

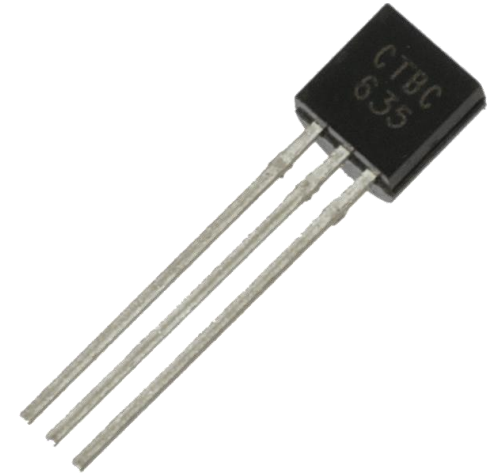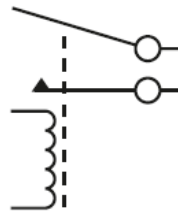

MULTIMETER

- ✚ Device used to test various electrical properties of a component or a circuit.
- ✚ Debugging Tool



REFERENCES

✚ [1] Dan O'Sullivan, Tom Igoe (2004)
Physical Computing: Sensing and Controlling the Physical World with Computers,
Thomson

✚ [2] Erik Brunvand. 2013.
Lights! speed! action!: fundamentals of physical computing for programmers.

Websites:

✚ [3] - <http://www.qldscienceteachers.com/junior-science/physics/electricity>

✚ [4] -
http://www.reddit.com/r/explainlikeimfive/comments/1qrdc9/eli5how_do_digital_devices_know_how_much_energy/